



Звіт

з лабораторної роботи №3

з дисципліни: “Моделювання комп’ютерних систем”

на тему: “Поведінковий опис цифрового автомата. Перевірка роботи автомата
за допомогою стенда Elbert V2 - Spartan 3A FPGA.”

Варіант №5

Виконав: ст.гр. КІ-201


Давида В.Р.

Прийняв:
Козак Н.Б.

Мета роботи:

На базі стенда Elbert V2 - Spartan 3A FPGA реалізувати цифровий автомат для обчислення значення виразу дотримуючись наступних вимог:

1. Функціонал пристрою повинен бути реалізований згідно отриманого варіанту завдання. Дивись розділ ЗАВДАННЯ.
2. Пристрій повинен бути ітераційним (АЛП (ALU) повинен виконувати за один такт одну операцію), та реалізованим згідно наступної структурної схеми (Малюнок 1).

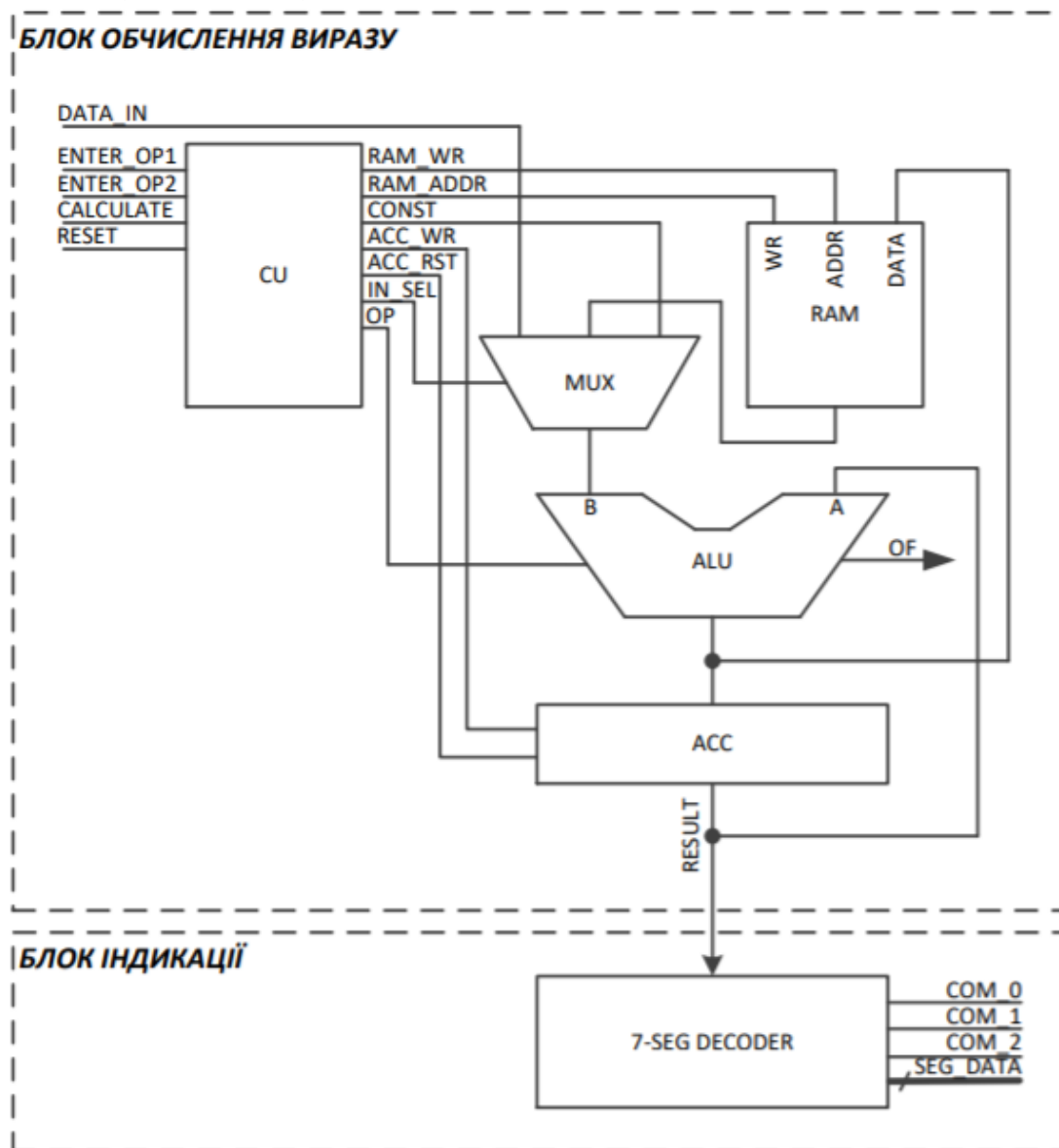

Малюнок 1 - Структурна схема автомата.

Завдання:


ВАРІАНТ	ВИРАЗ
<u>5</u>	$((1 \ll OP1) + OP2) - OP1$

Виконання:

1) Створив файл MUX.vhd і реалізував у ньому мультиплексор MUX (рис.1).

```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity my_MuX_intf is
5  port(
6      DATA_IN          : in  std_logic_vector(7 downto 0);
7      IN_SEL             : in  std_logic_vector(1 downto 0);
8      CONSTANT_BUS      : in  std_logic_vector(7 downto 0);
9      RAM_DATA_OUT_BUS  : in  std_logic_vector(7 downto 0);
10     IN_SEL_OUT_BUS     : out std_logic_vector(7 downto 0)
11 );
12 end my_MuX_intf;
13
14 architecture my_MuX_arch of my_MuX_intf is
15
16 begin
17     INSEL_A_MUX : process(DATA_IN, CONSTANT_BUS, RAM_DATA_OUT_BUS, IN_SEL)
18     begin
19         if(IN_SEL = "00") then
20             IN_SEL_OUT_BUS <= DATA_IN;
21         elsif(IN_SEL = "01") then
22             IN_SEL_OUT_BUS <= RAM_DATA_OUT_BUS;
23         else
24             IN_SEL_OUT_BUS <= CONSTANT_BUS;
25         end if;
26     end process INSEL_A_MUX;
27 end my_MuX_arch;
28
```

Рис.1. Реалізація мультиплексора у файлі MUX.vhd

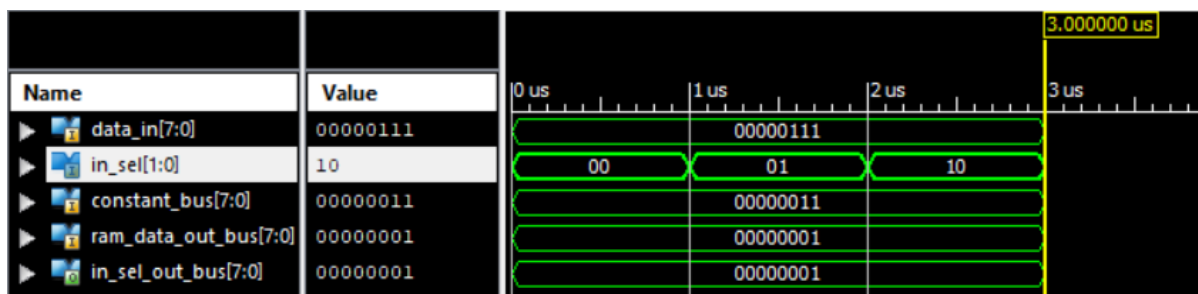

Симуляція роботи мультиплексора.


2) Створив файл ACC.vhd і реалізував у ньому регістр ACC (рис.2).

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4
5  entity my_ACC_intf is
6  port(
7      CLOCK          : in  std_logic;
8      ACC_WR         : in  std_logic;
9      ACC_RST        : in  std_logic;
10     ACC_DATA_IN_BUS : in  std_logic_vector(7 downto 0);
11     ACC_DATA_OUT_BUS : out std_logic_vector(7 downto 0)
12 );
13 end my_ACC_intf;
14
15 architecture my_ACC_arch of my_ACC_intf is
16
17     signal ACC_DATA : std_logic_vector(7 downto 0);
18
19     begin
20
21     ACC : process(CLOCK, ACC_DATA)
22     begin
23         if (rising_edge(CLOCK)) then
24             if (ACC_RST = '1') then
25                 ACC_DATA <= "00000000";
26             elsif (ACC_WR = '1') then
27                 ACC_DATA <= ACC_DATA_IN_BUS;
28             end if;
29         end if;
30         ACC_DATA_OUT_BUS <= ACC_DATA;
31     end process ACC;
32
33 end my_ACC_arch;
34

```

Рис.2. Реалізація регістра ACC у файлі ACC.vhd

 

Симуляція роботи регістра.


- 3) Визначив набір необхідних операцій для виконання виразу згідно свого варіанту і реалізував АЛП(ALU) у файлі ALU.vhd з підтримкою визначеного набору операцій (рис.3).

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.NUMERIC_STD.ALL;
4  use IEEE.STD_LOGIC_UNSIGNED.ALL;
5
6  entity my_ALU_intf is
7  port(
8      OP_CODE_BUS      : in  std_logic_vector(1 downto 0);
9      IN_SEL_OUT_BUS   : in  std_logic_vector(7 downto 0);
10     ACC_DATA_OUT_BUS  : in  std_logic_vector(7 downto 0);
11     ACC_DATA_IN_BUS   : out std_logic_vector(7 downto 0)
12 );
13 end my_ALU_intf;
14
15 architecture my_ALU_arch of my_ALU_intf is
16
17 begin
18
19     ALU : process(OP_CODE_BUS, IN_SEL_OUT_BUS, ACC_DATA_OUT_BUS)
20         variable A : unsigned(7 downto 0);
21         variable B : unsigned(7 downto 0);
22     begin
23         A := unsigned(ACC_DATA_OUT_BUS);
24         B := unsigned(IN_SEL_OUT_BUS);
25
26         case(OP_CODE_BUS) is
27             when "00" => ACC_DATA_IN_BUS <= STD_LOGIC_VECTOR(B);
28             when "01" => ACC_DATA_IN_BUS <= STD_LOGIC_VECTOR(A + B);
29             when "10" => ACC_DATA_IN_BUS <= STD_LOGIC_VECTOR(A - B);
30             when "11" =>
31                 case(B) is
32                     when x"00" => ACC_DATA_IN_BUS <= STD_LOGIC_VECTOR(A sll 0);
33                     when x"01" => ACC_DATA_IN_BUS <= STD_LOGIC_VECTOR(A sll 1);
34                     when x"02" => ACC_DATA_IN_BUS <= STD_LOGIC_VECTOR(A sll 2);
35                     when x"03" => ACC_DATA_IN_BUS <= STD_LOGIC_VECTOR(A sll 3);
36                     when x"04" => ACC_DATA_IN_BUS <= STD_LOGIC_VECTOR(A sll 4);
37                     when x"05" => ACC_DATA_IN_BUS <= STD_LOGIC_VECTOR(A sll 5);
38                     when x"06" => ACC_DATA_IN_BUS <= STD_LOGIC_VECTOR(A sll 6);
39                     when x"07" => ACC_DATA_IN_BUS <= STD_LOGIC_VECTOR(A sll 7);
40                     when others => ACC_DATA_IN_BUS <= STD_LOGIC_VECTOR(A sll 0);
41                 end case;
42             when others => ACC_DATA_IN_BUS <= "00000000";
43         end case;
44     end process ALU;
45
46 end my_ALU_arch;

```

Рис.3. Реалізація АЛП(ALU) у файлі ALU.vhd з підтримкою визначеного набору операцій.

 

Симуляція роботи АЛП

- 4) Визначив множину станів і реалізував пристрій керування (CU) у файлі CU.vhd (рис.4.).


```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity my_CU_intf is
5  port(
6  CLOCK      : in std_logic;
7  ENTER_OP1  : in std_logic;
8  ENTER_OP2  : in std_logic;
9  CALCULATE  : in std_logic;
10 RESET      : in std_logic;
11
12 RAM_WR      : out std_logic;
13 RAM_ADDR_BUS : out std_logic_vector(1 downto 0);
14 CONSTANT_BUS : out std_logic_vector(7 downto 0);
15 ACC_WR      : out std_logic;
16 ACC_RST     : out std_logic;
17 IN_SEL      : out std_logic_vector(1 downto 0);
18 OP_CODE_BUS : out std_logic_vector(1 downto 0)
19 );
20 end my_CU_intf;
21
22 architecture my_CU_arch of my_CU_intf is
23
24     type cu_state_type is (cu_rst, cu_idle, cu_load_op1, cu_load_op2, cu_run_calc0, cu_run_calc1, cu_run_calc2, cu_run_calc3, cu_finish);
25     signal cu_cur_state : cu_state_type;
26     signal cu_next_state : cu_state_type;
27
28     begin
29     CONSTANT_BUS <= "00000001";
30
31     CU_SYNC_PROC: process (CLOCK)
32     begin
33         if (rising_edge(CLOCK)) then
34             if (RESET = '1') then
35                 cu_cur_state <= cu_rst;
36             else
37                 cu_cur_state <= cu_next_state;
38             end if;
39         end if;
40     end process;
41
42     CUNEXT_STATE_DECODE: process (cu_cur_state, ENTER_OP1, ENTER_OP2, CALCULATE)
43     begin
44         --declare default state for next_state to avoid latches
45         cu_next_state <= cu_cur_state; --default is to stay in current state
46         --insert statements to decode next_state
47         --below is a simple example
48         case(cu_cur_state) is
49             when cu_rst =>
50                 cu_next_state <= cu_idle;
51             when cu_idle =>
52                 if (ENTER_OP1 = '1') then
53                     cu_next_state <= cu_load_op1;
54                 elsif (ENTER_OP2 = '1') then
55                     cu_next_state <= cu_load_op2;
56                 elsif (CALCULATE = '1') then
57                     cu_next_state <= cu_run_calc0;
58                 else
59                     cu_next_state <= cu_idle;
60                 end if;
61             when cu_load_op1 =>
62                 cu_next_state <= cu_idle;
63             when cu_load_op2 =>
64                 cu_next_state <= cu_idle;
65             when cu_run_calc0 =>
66                 cu_next_state <= cu_run_calc1;
67             when cu_run_calc1 =>
68                 cu_next_state <= cu_run_calc2;
69             when cu_run_calc2 =>
70                 cu_next_state <= cu_run_calc3;
71             when cu_run_calc3 =>
72                 cu_next_state <= cu_finish;
73             when cu_finish =>
74                 cu_next_state <= cu_finish;
75             when others =>
76                 cu_next_state <= cu_idle;
77         end case;
78     end process;
```

```

81  CU_OUTPUT_DECODE: process (cu_cur_state)
82  begin
83      case(cu_cur_state) is
84          when cu_rst =>
85              IN_SEL      <= "00";
86              OP_CODE_BUS <= "00";
87              RAM_ADDR_BUS <= "00";
88              RAM_WR      <= '0';
89              ACC_RST     <= '1';
90              ACC_WR      <= '0';
91          when cu_idle =>
92              IN_SEL      <= "00";
93              OP_CODE_BUS <= "00";
94              RAM_ADDR_BUS <= "00";
95              RAM_WR      <= '0';
96              ACC_RST     <= '0';
97              ACC_WR      <= '0';
98          when cu_load_op1 =>
99              IN_SEL      <= "00";
100             OP_CODE_BUS <= "00";
101             RAM_ADDR_BUS <= "00";
102             RAM_WR      <= '1';
103             ACC_RST     <= '0';
104             ACC_WR      <= '1';
105          when cu_load_op2 =>
106             IN_SEL      <= "00";
107             OP_CODE_BUS <= "00";
108             RAM_ADDR_BUS <= "01";
109             RAM_WR      <= '1';
110             ACC_RST     <= '0';
111             ACC_WR      <= '1';
112          when cu_run_calc0 =>
113             IN_SEL      <= "10";
114             OP_CODE_BUS <= "00";
115             RAM_ADDR_BUS <= "00";
116             RAM_WR      <= '0';
117             ACC_RST     <= '0';
118             ACC_WR      <= '1';
119          when cu_run_calc1 =>
120             IN_SEL      <= "01";
121             OP_CODE_BUS <= "11";
122             RAM_ADDR_BUS <= "00";
123             RAM_WR      <= '0';
124             ACC_RST     <= '0';
125             ACC_WR      <= '1';
126          when cu_run_calc2 =>
127             IN_SEL      <= "01";
128             OP_CODE_BUS <= "01";
129             RAM_ADDR_BUS <= "01";
130             RAM_WR      <= '0';
131             ACC_RST     <= '0';
132             ACC_WR      <= '1';
133          when cu_run_calc3 =>
134             IN_SEL      <= "01";
135             OP_CODE_BUS <= "10";
136             RAM_ADDR_BUS <= "00";
137             RAM_WR      <= '0';
138             ACC_RST     <= '0';
139             ACC_WR      <= '1';
140          when cu_finish =>
141             IN_SEL      <= "00";
142             OP_CODE_BUS <= "00";
143             RAM_ADDR_BUS <= "00";
144             RAM_WR      <= '0';
145             ACC_RST     <= '0';
146             ACC_WR      <= '0';
147          when others =>
148             IN_SEL      <= "00";
149             OP_CODE_BUS <= "00";
150             RAM_ADDR_BUS <= "00";
151             RAM_WR      <= '0';
152             ACC_RST     <= '0';
153             ACC_WR      <= '0';
154      end case;
155  end process;
156  end my_CU_arch;
157

```

Рис.4. Реалізація пристрою керування (CU) у файлі CU.vhd

 

Симуляція роботи керуючого автомата


- 5) Створив файл RAM.vhd і реалізував у ньому пам'ять пристрою (RAM) (рис.5).

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.STD_LOGIC_UNSIGNED.ALL;
4
5  entity my_RAM_intf is
6  port (
7      CLOCK          : in  std_logic;
8      RAM_WR          : in  std_logic;
9      RAM_ADDR_BUS    : in  STD_LOGIC_VECTOR(1 downto 0);
10     RAM_DATA_IN_BUS  : in  STD_LOGIC_VECTOR(7 downto 0);
11     RAM_DATA_OUT_BUS : out STD_LOGIC_VECTOR(7 downto 0)
12 );
13 end my_RAM_intf;
14
15 architecture my_RAM_arch of my_RAM_intf is
16
17     type ram_type is array (3 downto 0) of STD_LOGIC_VECTOR(7 downto 0);
18     signal RAM_UNIT          : ram_type;
19
20     begin
21         --when reset will init const
22         RAM : process(CLOCK, RAM_ADDR_BUS, RAM_UNIT)
23         begin
24             if (rising_edge(CLOCK)) then
25                 if (RAM_WR = '1') then
26                     RAM_UNIT(conv_integer(RAM_ADDR_BUS)) <= RAM_DATA_IN_BUS;
27                 end if;
28             end if;
29             RAM_DATA_OUT_BUS <= RAM_UNIT(conv_integer(RAM_ADDR_BUS));
30         end process RAM;
31
32     end my_RAM_arch;
33

```

Рис.5. Реалізація пам'яті пристрою (RAM) у файлі RAM.vhd

 

Симуляція роботи RAM

- б) Створив файл OUT_PUT_DECODER.vhd і реалізував в ньому блок індикації (7-SEG DECODER) (рис.6).

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.NUMERIC_STD.ALL;
4  use IEEE.STD_LOGIC_UNSIGNED.ALL;
5
6  entity OUT_PUT_DECODER_intf is
7  port(
8  CLOCK          : IN STD_LOGIC;
9  RESET          : IN STD_LOGIC;
10 ACC_DATA_OUT_BUS : IN std_logic_vector(7 downto 0);
11
12 COMM_ONES       : OUT STD_LOGIC;
13 COMM_DECS       : OUT STD_LOGIC;
14 COMM_HUNDREDS   : OUT STD_LOGIC;
15 SEG_A           : OUT STD_LOGIC;
16 SEG_B           : OUT STD_LOGIC;
17 SEG_C           : OUT STD_LOGIC;
18 SEG_D           : OUT STD_LOGIC;
19 SEG_E           : OUT STD_LOGIC;
20 SEG_F           : OUT STD_LOGIC;
21 SEG_G           : OUT STD_LOGIC;
22 DP              : OUT STD_LOGIC
23 );
24 end OUT_PUT_DECODER_intf;
25
26 architecture OUT_PUT_DECODER_arch of OUT_PUT_DECODER_intf is
27 signal ONES_BUS : STD_LOGIC_VECTOR(3 downto 0) := "0000";
28 signal DECS_BUS : STD_LOGIC_VECTOR(3 downto 0) := "0001";
29 signal HONDREDS_BUS : STD_LOGIC_VECTOR(3 downto 0) := "0000";
30
31 begin
32
33     BIN_TO_BCD : process (ACC_DATA_OUT_BUS)
34         variable hex_src : STD_LOGIC_VECTOR(7 downto 0) ;

```

```

35     variable bcd      : STD_LOGIC_VECTOR(11 downto 0) ;
36 begin
37     bcd      := (others => '0') ;
38     hex_src  := ACC_DATA_OUT_BUS;
39
40     for i in hex_src'range loop
41         if bcd(3 downto 0) > "0100" then
42             bcd(3 downto 0) := bcd(3 downto 0) + "0011" ;
43         end if ;
44         if bcd(7 downto 4) > "0100" then
45             bcd(7 downto 4) := bcd(7 downto 4) + "0011" ;
46         end if ;
47         if bcd(11 downto 8) > "0100" then
48             bcd(11 downto 8) := bcd(11 downto 8) + "0011" ;
49         end if ;
50
51         bcd := bcd(10 downto 0) & hex_src(hex_src'left) ; -- shift bcd + 1 new entry
52         hex_src := hex_src(hex_src'left - 1 downto hex_src'right) & '0' ; -- shift src + pad with 0
53     end loop ;
54
55     HONDREDS_BUS    <= bcd (11 downto 8);
56     DECS_BUS        <= bcd (7  downto 4);
57     ONES_BUS        <= bcd (3  downto 0);
58
59 end process BIN_TO_BCD;
60
61 INDICATE : process(CLOCK)
62     type DIGIT_TYPE is (ONES, DECS, HUNDREDS);
63
64     variable CUR_DIGIT    : DIGIT_TYPE := ONES;
65     variable DIGIT_VAL    : STD_LOGIC_VECTOR(3 downto 0) := "0000";
66     variable DIGIT_CTRL   : STD_LOGIC_VECTOR(6 downto 0) := "00000000";
67     variable COMMONS_CTRL : STD_LOGIC_VECTOR(2 downto 0) := "000";
68
69     begin
70         if (rising_edge(CLOCK)) then
71             if(RESET = '0') then
72                 case CUR_DIGIT is
73                     when ONES =>
74                         DIGIT_VAL := ONES_BUS;
75                         CUR_DIGIT := DECS;
76                         COMMONS_CTRL := "001";
77                     when DECS =>
78                         DIGIT_VAL := DECS_BUS;
79                         CUR_DIGIT := HUNDREDS;
80                         COMMONS_CTRL := "010";
81                     when HUNDREDS =>
82                         DIGIT_VAL := HONDREDS_BUS;
83                         CUR_DIGIT := ONES;
84                         COMMONS_CTRL := "100";
85                     when others =>
86                         DIGIT_VAL := ONES_BUS;
87                         CUR_DIGIT := ONES;
88                         COMMONS_CTRL := "000";
89                 end case;
90
91                 case DIGIT_VAL is
92                     when "0000" => DIGIT_CTRL := "1111110";
93                     when "0001" => DIGIT_CTRL := "01100000";
94                     when "0010" => DIGIT_CTRL := "1101101";
95                     when "0011" => DIGIT_CTRL := "1111001";
96                     when "0100" => DIGIT_CTRL := "0110011";
97                     when "0101" => DIGIT_CTRL := "1011011";
98                     when "0110" => DIGIT_CTRL := "1011111";
99                     when "0111" => DIGIT_CTRL := "11100000";
100                    when "1000" => DIGIT_CTRL := "1111111";
101                    when "1001" => DIGIT_CTRL := "1111011";
102                    when others => DIGIT_CTRL := "00000000";

```

```

103         end case;
104     else
105         DIGIT_VAL := ONES_BUS;
106         CUR_DIGIT := ONES;
107         COMMONS_CTRL := "000";
108     end if;
109
110     COMM_ONES    <= COMMONS_CTRL(0);
111     COMM_DECS    <= COMMONS_CTRL(1);
112     COMM_HUNDREDS <= COMMONS_CTRL(2);
113
114     SEG_A <= DIGIT_CTRL(6);
115     SEG_B <= DIGIT_CTRL(5);
116     SEG_C <= DIGIT_CTRL(4);
117     SEG_D <= DIGIT_CTRL(3);
118     SEG_E <= DIGIT_CTRL(2);
119     SEG_F <= DIGIT_CTRL(1);
120     SEG_G <= DIGIT_CTRL(0);
121     DP    <= '0';
122
123     end if;
124 end process INDICATE;
125
126
127 end OUT_PUT_DECODER_arch;
128
129

```

Рис.6. Реалізація блоку індикації (7-SEG DECODER) в файлі
OUT_PUT_DECODER.vhd

- 7) Згенерував символи для імплементованих компонентів і створив схему у файлі Top_level.sch (рис.7).

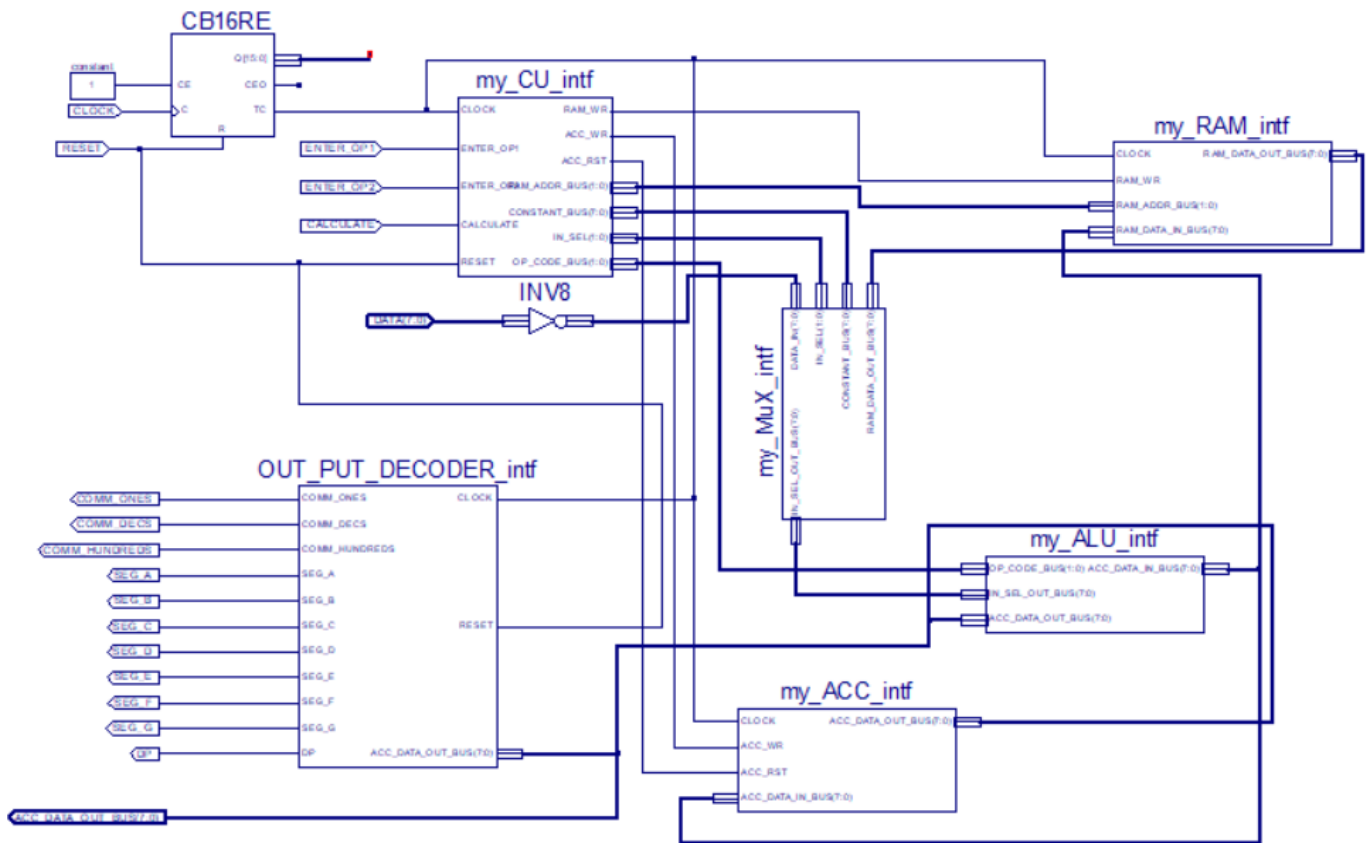


Рис.7. Схема з використанням імплементованих компонентів

8) Test bench *TB_TOPLEVEL.vhd*.

```

1  LIBRARY ieee;
2  USE ieee.std_logic_1164.ALL;
3  USE ieee.numeric_std.ALL;
4  LIBRARY UNISIM;
5  USE UNISIM.Vcomponents.ALL;
6  ENTITY TOP_LEVEL_TOP_LEVEL_sch_tb IS
7  END TOP_LEVEL_TOP_LEVEL_sch_tb;
8  ARCHITECTURE behavioral OF TOP_LEVEL_TOP_LEVEL_sch_tb IS
9
10     COMPONENT TOP_LEVEL
11     PORT( RESET      : IN STD_LOGIC;
12           CLOCK      : IN STD_LOGIC;
13           ENTER_OP1   : IN STD_LOGIC;
14           ENTER_OP2   : IN STD_LOGIC;
15           CALCULATE   : IN STD_LOGIC;
16           DATA       : IN STD_LOGIC_VECTOR (7 DOWNTO 0);
17           COMM_ONES    : OUT  STD_LOGIC;
18           COMM_DECS    : OUT  STD_LOGIC;
19           COMM_HUNDREDS : OUT  STD_LOGIC;
20           SEG_A       : OUT  STD_LOGIC;
21           SEG_B       : OUT  STD_LOGIC;
22           SEG_C       : OUT  STD_LOGIC;
23           SEG_D       : OUT  STD_LOGIC;
24           SEG_E       : OUT  STD_LOGIC;
25           SEG_F       : OUT  STD_LOGIC;
26           SEG_G       : OUT  STD_LOGIC;
27           DP          : OUT  STD_LOGIC;
28           ACC_DATA_OUT_BUS : OUT STD_LOGIC_VECTOR(7 DOWNTO 0));
29     END COMPONENT;
30
31     signal op1 : STD_LOGIC_VECTOR(7 DOWNTO 0);
32     signal op2 : STD_LOGIC_VECTOR(7 DOWNTO 0);
33     signal RESET      : STD_LOGIC;
34     signal CLOCK      : STD_LOGIC;
35
36     signal ENTER_OP1 : STD_LOGIC;
37     signal ENTER_OP2 : STD_LOGIC;
38     signal CALCULATE : STD_LOGIC;
39     signal DATA : STD_LOGIC_VECTOR (7 DOWNTO 0);
40     signal COMM_ONES : STD_LOGIC;
41     signal COMM_DECS : STD_LOGIC;
42     signal COMM_HUNDREDS : STD_LOGIC;
43     signal SEG_A : STD_LOGIC;
44     signal SEG_B : STD_LOGIC;
45     signal SEG_C : STD_LOGIC;
46     signal SEG_D : STD_LOGIC;
47     signal SEG_E : STD_LOGIC;
48     signal SEG_F : STD_LOGIC;
49     signal SEG_G : STD_LOGIC;
50     signal DP : STD_LOGIC;
51     signal ACC_DATA_OUT_BUS : STD_LOGIC_VECTOR(7 DOWNTO 0);
52
53     constant CLK_period: time := 1 us;
54     constant TC_period: time := 65536 us;
55
56
57
58 BEGIN
59
60     UUT: TOP_LEVEL PORT MAP(
61     RESET => RESET,
62     CLOCK => CLOCK,
63     ENTER_OP1 => ENTER_OP1,
64     ENTER_OP2 => ENTER_OP2,
65     CALCULATE => CALCULATE,
66     DATA => DATA,
67     COMM_ONES => COMM_ONES,
68     COMM_DECS => COMM_DECS,

```

```

69     COMM_HUNDREDS => COMM_HUNDREDS,
70     SEG_A => SEG_A,
71     SEG_B => SEG_B,
72     SEG_C => SEG_C,
73     SEG_D => SEG_D,
74     SEG_E => SEG_E,
75     SEG_F => SEG_F,
76     SEG_G => SEG_G,
77     DP => DP,
78     ACC_DATA_OUT_BUS => ACC_DATA_OUT_BUS
79
80 );
81
82 CLK_process : process
83 begin
84     CLOCK <= '1';
85     wait for CLK_period/2;
86     CLOCK <= '0';
87     wait for CLK_period/2;
88 end process CLK_process;
89
90
91
92 stim_proc: process
93 begin
94     RESET <= '1';
95     ENTER_OP1 <= '0';
96     ENTER_OP2 <= '0';
97     CALCULATE <= '0';
98     DATA <=(others => '0');
99
100     wait for 2*CLK_period;
101     RESET <='0';
102
103     wait for 4*TC_period;
104     ENTER_OP1 <='1';
105     DATA <= op1;
106
107     wait for 2*TC_period;
108     ENTER_OP1 <='0';
109
110     wait for 4*TC_period;
111     ENTER_OP2 <='1';
112     DATA <= op2;
113
114     wait for 2*TC_period;
115     ENTER_OP2 <='0';
116     wait for 4*TC_period;
117
118     CALCULATE <= '1';
119     wait for 8*TC_period;
120     wait;
121 end process stim_proc; --1.835 s
122 END;
123

```


9) Constraints

```

1  #*****
2  #                               UCF for ElbertV2 Development Board
3  #*****
4  CONFIG VCCAUX = "3.3" ;
5
6  # Clock 12 MHz
7  NET "CLOCK"                LOC = P129 | IOSTANDARD = LVCMOS33 | PERIOD = 12MHz;
8
9  #*****
10 #                               Seven Segment Display
11 #*****
12
13 NET "SEG_A"      LOC = P117 | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
14 NET "SEG_B"      LOC = P116 | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
15 NET "SEG_C"      LOC = P115 | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
16 NET "SEG_D"      LOC = P113 | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
17 NET "SEG_E"      LOC = P112 | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
18 NET "SEG_F"      LOC = P111 | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
19 NET "SEG_G"      LOC = P110 | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
20 NET "DP"         LOC = P114 | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
21
22 NET "COMM_HUNDREDS" LOC = P124 | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
23 NET "COMM_DECS"    LOC = P121 | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
24 NET "COMM_ONES"    LOC = P120 | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
25 #*****
26 #                               DP Switches
27 #*****
28
29 NET "DATA(0)"      LOC = P70 | PULLUP | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
30 NET "DATA(1)"      LOC = P69 | PULLUP | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
31 NET "DATA(2)"      LOC = P68 | PULLUP | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
32 NET "DATA(3)"      LOC = P64 | PULLUP | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
33 NET "DATA(4)"      LOC = P63 | PULLUP | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
34 NET "DATA(5)"      LOC = P60 | PULLUP | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
35 NET "DATA(6)"      LOC = P59 | PULLUP | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
36 NET "DATA(7)"      LOC = P58 | PULLUP | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
37
38 #*****
39 #                               Switches
40 #*****
41
42 NET "ENTER_OP1"     LOC = P80 | PULLUP | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
43 NET "ENTER_OP2"     LOC = P79 | PULLUP | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
44 NET "CALCULATE"     LOC = P78 | PULLUP | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
45 NET "RESET"         LOC = P75 | PULLUP | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
46

```

 


Рис.8. Часова діаграма згідно методичних вказівок

Перевірка:

$((1 \ll OP1) + OP2) - OP1$

$OP1 \Rightarrow 1$

$OP2 \Rightarrow 1$


$((1 \ll 1) + 1) - 1$

$1 \ll 1 = 2$

$2 + 1 = 3$

$3 - 1 = 2_{10} = 00000010_2$

 В результаті на всі сегменти окрім c та f подалася одиниця, тобто число 2



7-сегментний індикатор.

Висновок:

На цій лабораторній роботі реалізував цифровий автомат для обчислення значення виразу та симулював його роботу.